

$$\textcircled{1} \frac{V_o}{V_i} = \frac{\frac{1}{RCj\omega}}{\frac{1}{RCj\omega} + R} = \boxed{\frac{1}{1+RCj\omega}}$$

$$\textcircled{2} \left| \frac{V_o}{V_i} \right| = \frac{\sqrt{(1)^2}}{\sqrt{1^2 + (RC\omega)^2}} = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$

$$\left| \frac{V_o}{V_i} \right|_{2\text{kHz}} = \frac{1}{\sqrt{1 + [(1000\Omega)(1 \times 10^{-6}\text{F})(2\pi \cdot 2000 \text{ cycles/sec})]^2}}$$

$$= \frac{1}{\sqrt{1 + [4\pi]^2}} = \frac{1}{\sqrt{158.9}} = \boxed{0.079}$$

$$\textcircled{3} \angle \frac{V_o}{V_i} \Big|_{2\text{kHz}} = -\text{TAN}^{-1}(RC\omega) = -\text{TAN}^{-1}(1000\Omega \cdot 1 \times 10^{-6}\text{F} \cdot 2\pi \cdot 2000\text{Hz})$$

$$= -\text{TAN}^{-1}(4\pi) = \boxed{-85.4^\circ}$$

$$\textcircled{4} -10\text{dB} \Rightarrow 20 \text{LOG} \left| \frac{V_o}{V_i} \right| = -10\text{dB}$$

$$\therefore \left| \frac{V_o}{V_i} \right| = 10^{\left[\frac{-10}{20} \right]} = 10^{-0.5} = 0.316$$

$$0.316 = \frac{1}{\sqrt{1 + [(1000\Omega)(1 \times 10^{-6}\text{F})(2\pi \cdot \omega)]^2}} \Rightarrow \omega = \boxed{}$$

SOLVE

$$\textcircled{5} \omega_c = \frac{1}{RC} = \frac{1}{1000\Omega \cdot 1 \times 10^{-6}\text{F}} = \frac{1}{0.001} = \boxed{1000 \text{ RAD/S}}$$

$$f_c = \frac{\omega_c}{2\pi} = \frac{1000 \text{ RAD/S}}{2\pi} = \boxed{159.2 \text{ HZ}}$$