
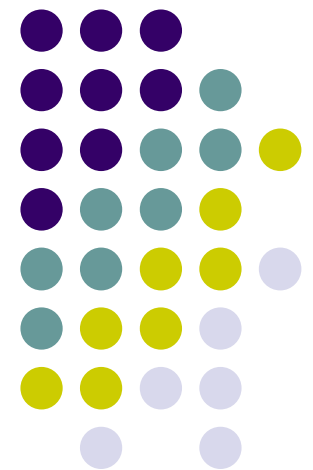


Transmission Line Theory


EE142
Dr. Ray Kwok

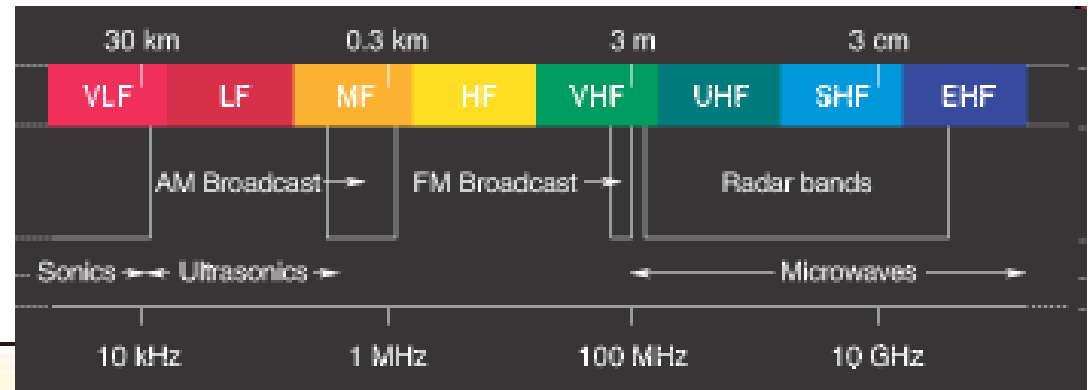


RF Spectrum





THE ELECTROMAGNETIC SPECTRUM

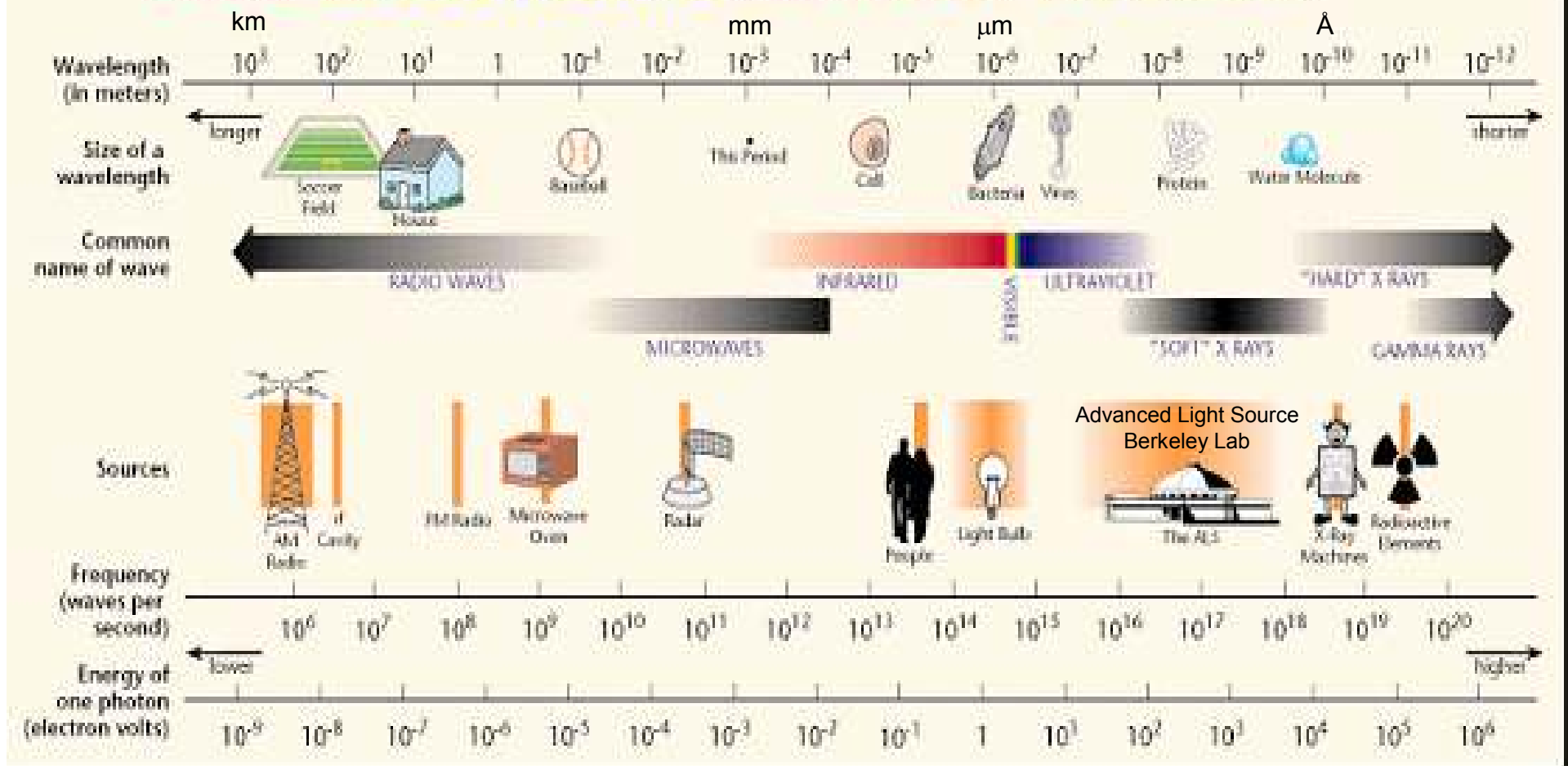

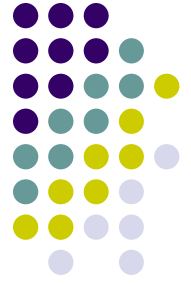


RF / Microwave Circuit

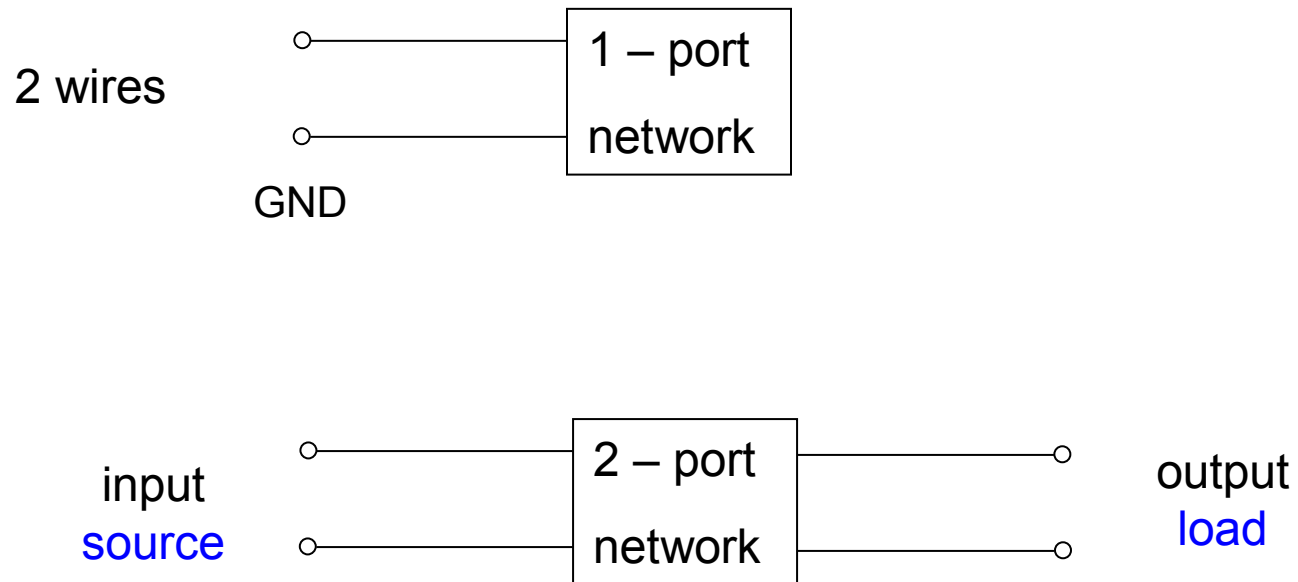

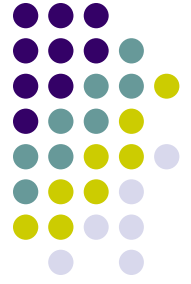


Series connection

low f

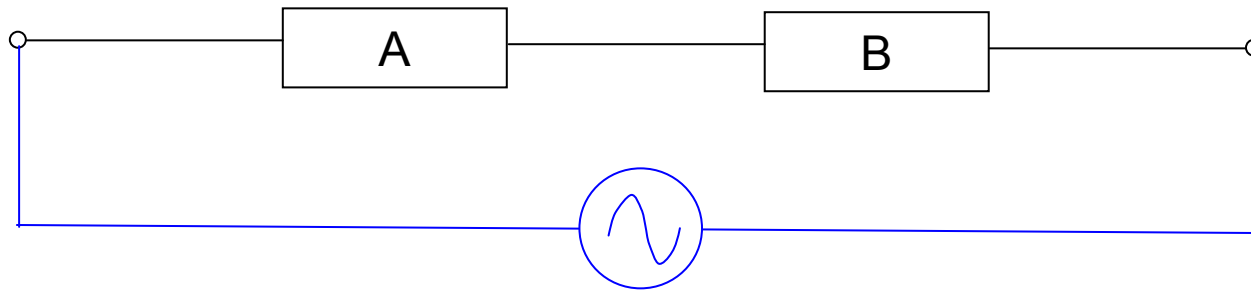


RF

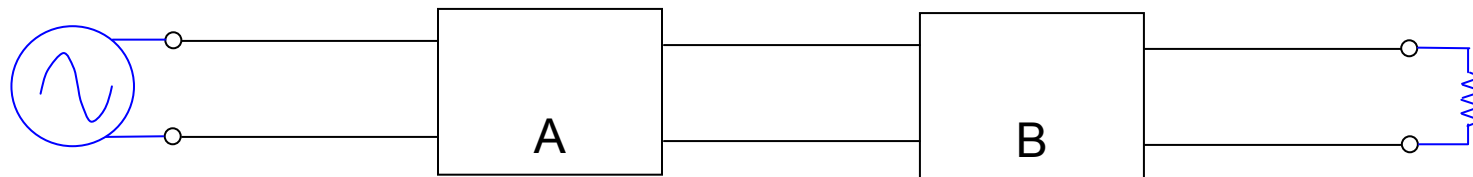




Parallel connection

low f

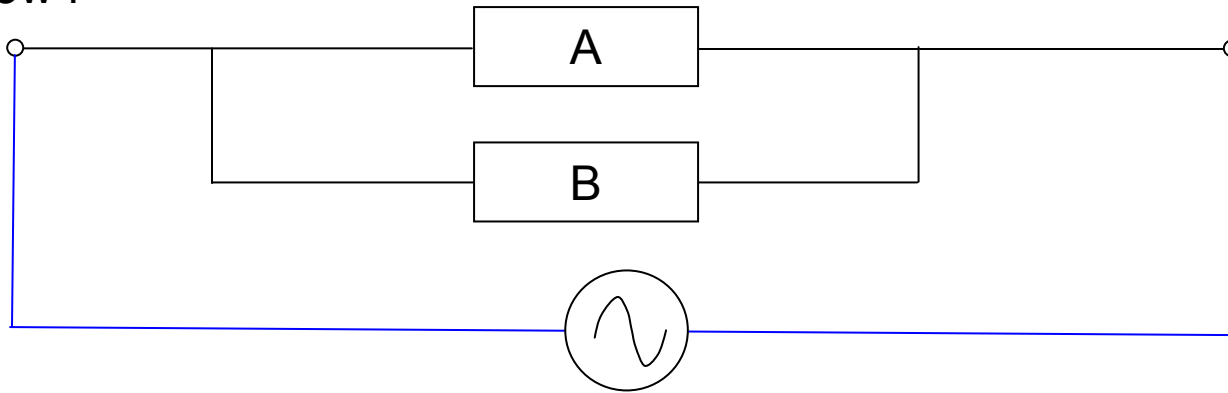

RF

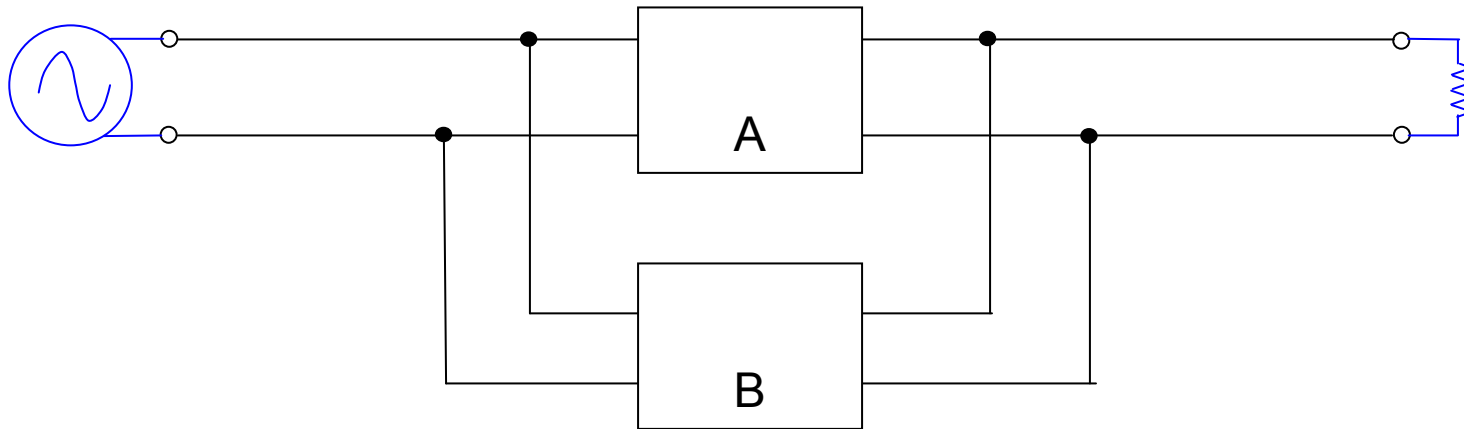



Common transmission lines





most correct schematic




twisted pair
VLF
lossy & noisy

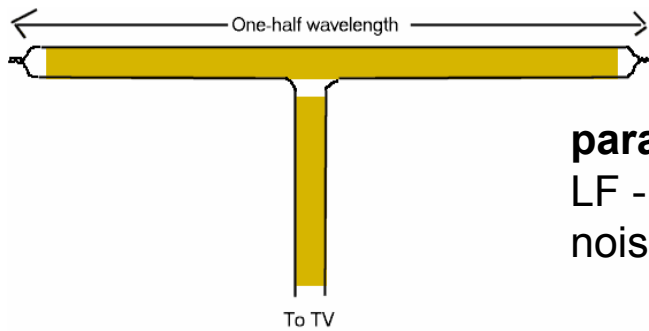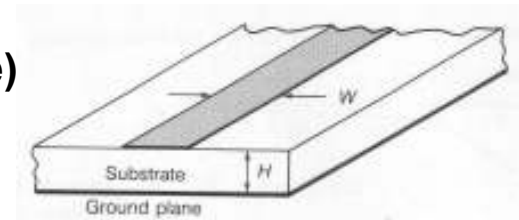microstrip (line)
no distortion
wide freq range
lowest cost




parallel wire
LF - HF
noisy & lossy

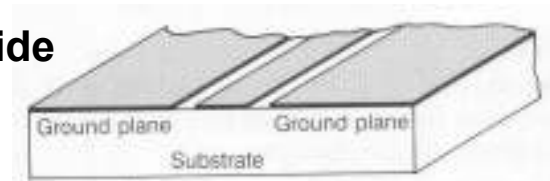
co-planar waveguide
low cost
flip chip access
complex design




coaxial cable
no distortion
wide freq range

waveguide
lowest loss
freq bands

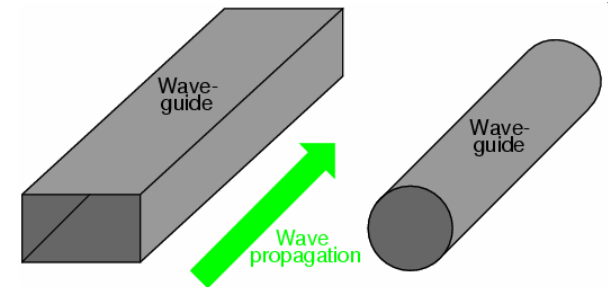

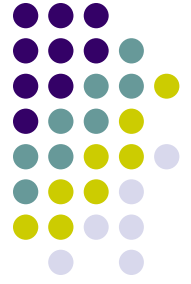

Equivalent circuit

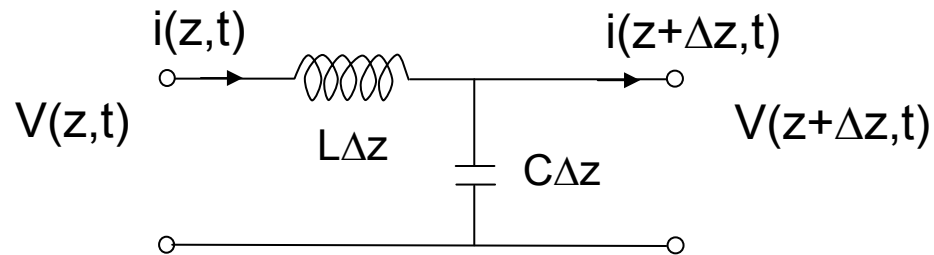

Ideal transmission line


Kirchhoff's law: $V(z, t) - (L\Delta z) \frac{\partial i(z, t)}{\partial t} = V(z + \Delta z, t) \approx V(z, t) + \frac{\partial V(z, t)}{\partial z} \Delta z$ Taylor

$$\boxed{-L \frac{\partial i(z, t)}{\partial t} = \frac{\partial V(z, t)}{\partial z}}$$

Junction rule: $i(z + \Delta z, t) - i(z, t) = -(C\Delta z) \frac{\partial V(z, t)}{\partial t} \approx \frac{\partial i(z, t)}{\partial z} \Delta z$

$Q = CV$
 $dQ/dt = i = C dV/dt$
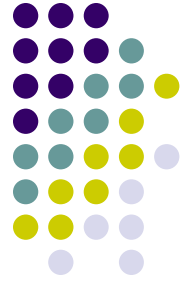
$$\boxed{-C \frac{\partial V(z, t)}{\partial t} = \frac{\partial i(z, t)}{\partial z}}$$



Coupled equations (V – i)

$$-L \frac{\partial i(z, t)}{\partial t} = \frac{\partial V(z, t)}{\partial z}$$

$$-C \frac{\partial V(z, t)}{\partial t} = \frac{\partial i(z, t)}{\partial z}$$

$$-L \frac{\partial^2 i}{\partial t^2} = \frac{\partial^2 V}{\partial t \partial z} = \frac{\partial}{\partial z} \left(-\frac{1}{C} \frac{\partial i}{\partial z} \right) = -\frac{1}{C} \frac{\partial^2 i}{\partial z^2}$$

$$\frac{\partial^2 i}{\partial z^2} = LC \frac{\partial^2 i}{\partial t^2} \quad \text{current wave}$$

similarly

$$-C \frac{\partial^2 V}{\partial t^2} = \frac{\partial^2 i}{\partial t \partial z} = \frac{\partial}{\partial z} \left(-\frac{1}{L} \frac{\partial V}{\partial z} \right) = -\frac{1}{L} \frac{\partial^2 V}{\partial z^2}$$

$$\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2} \quad \text{voltage wave}$$



Wave equation

$$f(x \pm vt) \equiv f(u)$$

reverse / forward traveling wave

$$\frac{\partial f}{\partial x} = f'(u) \frac{\partial u}{\partial x} = f'(u)$$

$$\frac{\partial^2 f}{\partial x^2} = f''(u) \frac{\partial u}{\partial x} = f''(u)$$

$$\frac{\partial f}{\partial t} = f'(u) \frac{\partial u}{\partial t} = \pm v f'(u)$$

$$\frac{\partial^2 f}{\partial t^2} = \pm v f''(u) \frac{\partial u}{\partial t} = v^2 f''(u)$$

$$\frac{\partial^2 f}{\partial x^2} = \frac{1}{v^2} \frac{\partial^2 f}{\partial t^2}$$

wave equation

note:

$$x \pm vt = \frac{1}{k} \left(\frac{2\pi}{\lambda} x \pm \frac{2\pi}{\lambda} vt \right)$$

$$= \frac{1}{k} (kx \pm 2\pi ft)$$

$$= \pm \frac{1}{k} (\omega t \pm kx)$$

$$f(x \pm vt) = f(\omega t \pm kx)$$

$$f(\omega t - \vec{k} \cdot \vec{r}) \quad (3D)$$



Voltage & Current Waves

$$V(z, t) = V_o^+ e^{j(\omega t - \beta z)} + V_o^- e^{j(\omega t + \beta z)}$$

$$i(z, t) = I_o^+ e^{j(\omega t - \beta z)} - I_o^- e^{j(\omega t + \beta z)}$$

where $\beta = \frac{2\pi}{\lambda}$

$$v = f\lambda = (2\pi f) \left(\frac{\lambda}{2\pi} \right) = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

why "-" ?

$$\frac{\partial i}{\partial z} = -j\beta I_o^+ e^{j(\omega t - \beta z)} - j\beta I_o^- e^{j(\omega t + \beta z)}$$

$$\frac{\partial i}{\partial z} = -C \frac{\partial V}{\partial t} = -C [j\omega V_o^+ e^{j(\omega t - \beta z)} + j\omega V_o^- e^{j(\omega t + \beta z)}]$$


$$\beta I_o^+ = C\omega V_o^+$$

$$\beta I_o^- = C\omega V_o^-$$

$$V_o^\pm = \frac{\beta}{C\omega} I_o^\pm = \frac{\sqrt{LC}}{C} I_o^\pm = \sqrt{\frac{L}{C}} I_o^\pm \equiv Z_o I_o^\pm$$

$$v = \frac{1}{\sqrt{LC}}$$

$$Z_o = \sqrt{\frac{L}{C}}$$

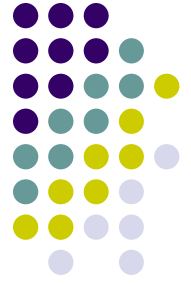

Fields and circuits

$$\nabla^2 \begin{pmatrix} \vec{E} \\ \vec{H} \end{pmatrix} = \mu\epsilon \frac{\partial^2}{\partial t^2} \begin{pmatrix} \vec{E} \\ \vec{H} \end{pmatrix}$$

$$\vec{E}(z, t) = \vec{E}_{oi} e^{j(\omega t - \vec{k}_i \cdot \vec{r})} + \vec{E}_{or} e^{j(\omega t - \vec{k}_r \cdot \vec{r})}$$

$$\vec{H}(z, t) = \vec{H}_{oi} e^{j(\omega t - \vec{k}_i \cdot \vec{r})} - \vec{H}_{or} e^{j(\omega t - \vec{k}_r \cdot \vec{r})}$$

$$v = \frac{1}{\sqrt{\mu\epsilon}}$$

$$\eta = \sqrt{\frac{\mu}{\epsilon}}$$


$$\frac{\partial^2}{\partial z^2} \begin{pmatrix} V \\ i \end{pmatrix} = LC \frac{\partial^2}{\partial t^2} \begin{pmatrix} V \\ i \end{pmatrix}$$

$$V(z, t) = V_o^+ e^{j(\omega t - \beta z)} + V_o^- e^{j(\omega t + \beta z)}$$

$$i(z, t) = I_o^+ e^{j(\omega t - \beta z)} - I_o^- e^{j(\omega t + \beta z)}$$

$$v = \frac{1}{\sqrt{LC}}$$

$$Z_o = \sqrt{\frac{L}{C}}$$

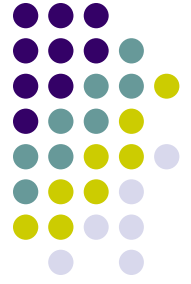


What is Z_0 ?

- Characteristic Impedance.
- 50 ohms for most communications system,
- 75 ohms for TV cable.
- Measure 75 ohms with a ohmmeter?
- Two 75Ω cables together (in series) makes a 150Ω cable?
- $75 + 75 = 75$!!!!
- What does Z_0 represent?



Reflection at Load

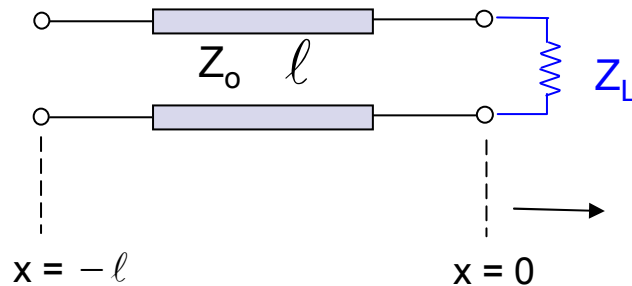

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

$$i(x) = I_o^+ e^{-j\beta x} - I_o^- e^{j\beta x}$$

$$V(0) \equiv V_L = V_o^+ + V_o^- \quad \text{at the load}$$

$$i(0) \equiv I_L = I_o^+ - I_o^- = \frac{1}{Z_o} (V_o^+ - V_o^-)$$

$$\frac{V_L}{I_L} \equiv Z_L = Z_o \left(\frac{V_o^+ + V_o^-}{V_o^+ - V_o^-} \right)$$

$$Z_L (V_o^+ - V_o^-) = Z_o (V_o^+ + V_o^-)$$

$$V_o^+ (Z_L - Z_o) = V_o^- (Z_L + Z_o)$$

$$\frac{V_o^-}{V_o^+} \equiv \Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$Z_L \neq Z_o$
reflection

Define normalized impedance

$$\bar{Z} \equiv \frac{Z}{Z_o}$$

$$\Gamma_L = \frac{\bar{Z}_L - 1}{\bar{Z}_L + 1}$$



Example

does it work?



75Ω




75Ω



50Ω

Impedance at Input

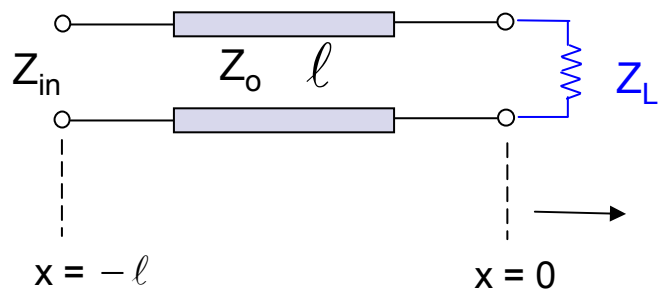

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

$$i(x) = I_o^+ e^{-j\beta x} - I_o^- e^{j\beta x}$$

$$Z_{in} \equiv \frac{V_{in}}{I_{in}} = \frac{V(-l)}{i(-l)} = \frac{V_o^+ e^{j\beta l} + V_o^- e^{-j\beta l}}{\frac{1}{Z_o} (V_o^+ e^{j\beta l} - V_o^- e^{-j\beta l})}$$

$$Z_{in} = Z_o \left(\frac{e^{j\beta l} + \Gamma_L e^{-j\beta l}}{e^{j\beta l} - \Gamma_L e^{-j\beta l}} \right)$$

$$\bar{Z}_{in} = \frac{e^{-j\beta l} \left(\frac{1 + j \tan \beta l}{1 - j \tan \beta l} \right) + \left(\frac{\bar{Z}_L - 1}{\bar{Z}_L + 1} \right) e^{-j\beta l}}{e^{-j\beta l} \left(\frac{1 + j \tan \beta l}{1 - j \tan \beta l} \right) - \left(\frac{\bar{Z}_L - 1}{\bar{Z}_L + 1} \right) e^{-j\beta l}}$$


$$\bar{Z}_{in} = \frac{(\bar{Z}_L + 1)(1 + j \tan \beta l) + (\bar{Z}_L - 1)(1 - j \tan \beta l)}{(\bar{Z}_L + 1)(1 + j \tan \beta l) - (\bar{Z}_L - 1)(1 - j \tan \beta l)}$$

$$\bar{Z}_{in} = \frac{2(\bar{Z}_L + j \tan \beta l)}{2(1 + j \bar{Z}_L \tan \beta l)}$$


$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$
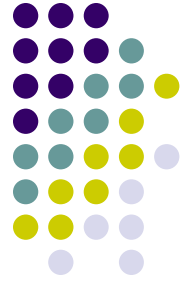
$$Z_{in} = Z_o \left(\frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$





Exercise

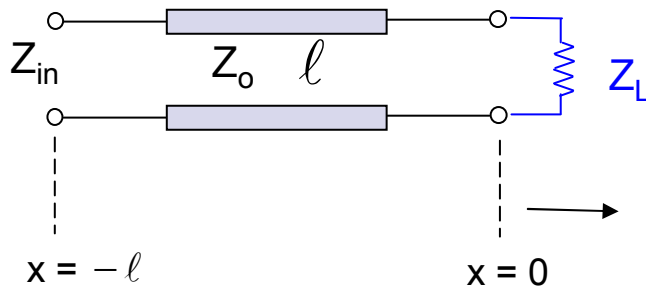

$$\begin{aligned} Z_o &= 50 \Omega \\ Z_L &= 100 \Omega \\ Z_{in} &= ? \end{aligned}$$

For length = $\lambda/8$? $\lambda/4$? $\lambda/2$?

What if $Z_o = Z_L = 50 \Omega$?

Would the length make any difference?

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$


$$Z_{in} = Z_o \left(\frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$50 \Omega \angle -37^\circ$$


$$25 \Omega$$

$$100 \Omega$$

$$Z_{in} = Z_o = Z_L$$

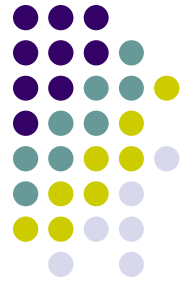

Transmission Line Impedance

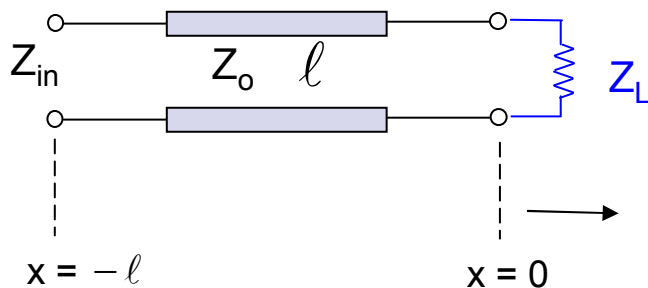

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$Z_{in} = Z_o \left(\frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

case 1: $\beta l = 0$, or $l = 0$

$$\tan \beta l = 0$$

$$Z_{in} = Z_L$$

case 2: $\beta l = \pi$, or $l = \lambda/2$

$$\tan \beta l = 0$$

$$Z_{in} = Z_L$$


case 3: $\beta l = \pi/2$, or $l = \lambda/4$

$$\tan \beta l \rightarrow \infty$$


$$Z_{in} = Z_o^2 / Z_L$$

Quarter-wave transformer (impedance),
real-to-real, complex-to-complex.

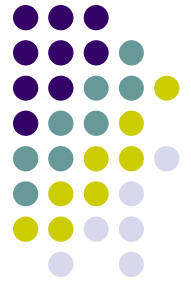note: at low freq, $\beta \rightarrow 0$, $Z_{in} = Z_L$ regardless of line length or line impedance.



Reflection at Input

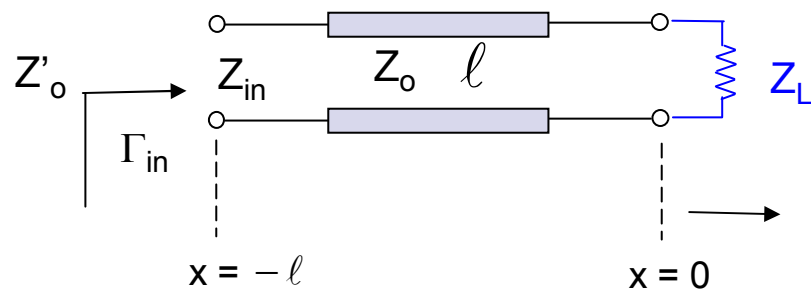

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$Z_{in} = Z_o \left(\frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$\Gamma_{in} = \frac{Z_{in} - Z'_o}{Z_{in} + Z'_o} = \frac{\bar{Z}'_{in} - 1}{\bar{Z}'_{in} + 1}$$


In general

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{\bar{Z}_{in} - 1}{\bar{Z}_{in} + 1}$$

just have to know what Z to use



Exercise

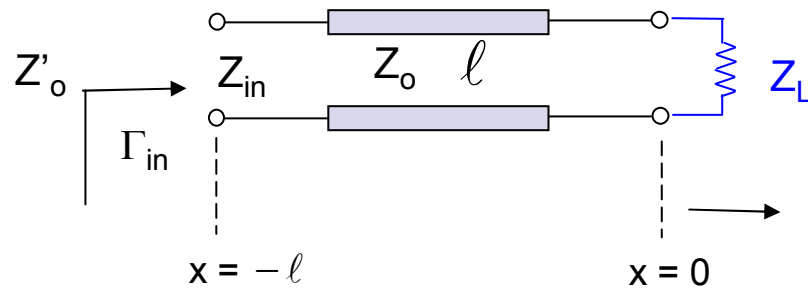

$$Z_o = 50 \Omega$$

$$Z'_o = 50 \Omega$$

$$Z_L = 100 \Omega$$

$$\text{Length} = \lambda/8$$

$$\Gamma_L = ? \quad \Gamma_{in} = ?$$

What if Z'_o is 75Ω ?

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$


$$Z_{in} = Z_o \left(\frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$\Gamma_{in} = \frac{Z_{in} - Z'_o}{Z_{in} + Z'_o} = \frac{\bar{Z}'_{in} - 1}{\bar{Z}'_{in} + 1}$$


$$1/3$$

$$1/3 (-90^\circ) \text{ only change phase !?!}$$

$$0.388 (235^\circ)$$

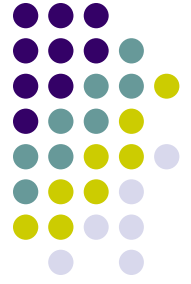

Voltage wave in transmission line

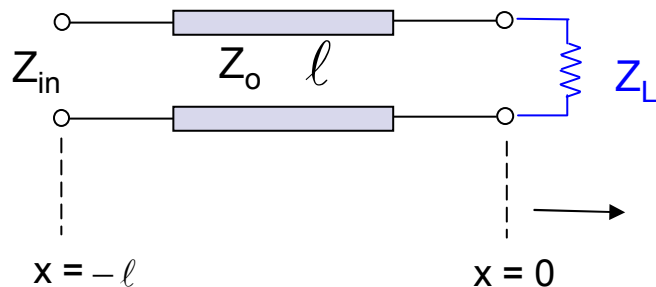

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

$$V(x) = V_o^+ e^{-j\beta x} (1 + \Gamma_L e^{2j\beta x})$$

$$|V| = |V_o^+| |1 + \Gamma_L e^{2j\beta x}|$$

$$\Gamma_L \equiv \rho e^{j\theta}$$

$$|V| = V_o^+ |1 + \rho e^{j(\theta + 2\beta x)}|$$

$$|V| = V_o^+ \sqrt{(1 + \rho \cos(\theta + 2\beta x))^2 + \rho^2 \sin^2(\theta + 2\beta x)}$$

$$|V| = V_o^+ \sqrt{1 + 2\rho \cos(\theta + 2\beta x) + \rho^2}$$

$$|V| = V_o^+ \sqrt{(1 + \rho)^2 - 2\rho(1 - \cos(\theta + 2\beta x))}$$

$$|V| = V_o^+ \sqrt{(1 + \rho)^2 - 4\rho \sin^2\left(\frac{\theta + 2\beta x}{2}\right)}$$

min when sine = 1


$$V_{\min} = V_o^+ \sqrt{(1 + \rho)^2 - 4\rho} = V_o^+ (1 - \rho)$$

max when sine = 0

$$V_{\max} = V_o^+ \sqrt{(1 + \rho)^2} = V_o^+ (1 + \rho)$$



Voltage Standing Wave

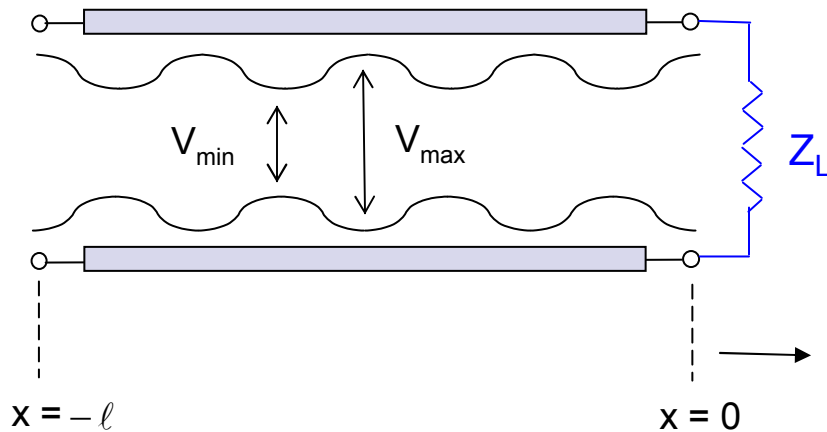

$$V(x) = V_o^+ e^{-j\beta x} + V_o^- e^{j\beta x}$$

standing wave

If $|V_o^+| = |V_o^-|$, $|\Gamma_L| \equiv \rho = \pm 1$
perfect standing wave with nodes

$$|V| = V_o^+ \sqrt{(1+\rho)^2 - 4\rho \sin^2\left(\frac{\theta + 2\beta x}{2}\right)}$$

$$\text{min when } \frac{\theta + 2\beta x}{2} = \pm \frac{(2n+1)\pi}{2}$$


$$(x < 0) \quad x = -\left[\theta \mp (2n+1)\pi\right] \frac{\lambda}{4\pi}$$

$$\text{max when } \frac{\theta + 2\beta x}{2} = \pm n\pi$$

$$x = -\left[\theta \mp 2n\pi\right] \frac{\lambda}{4\pi}$$



VSWR (Voltage Standing Wave Ratio)

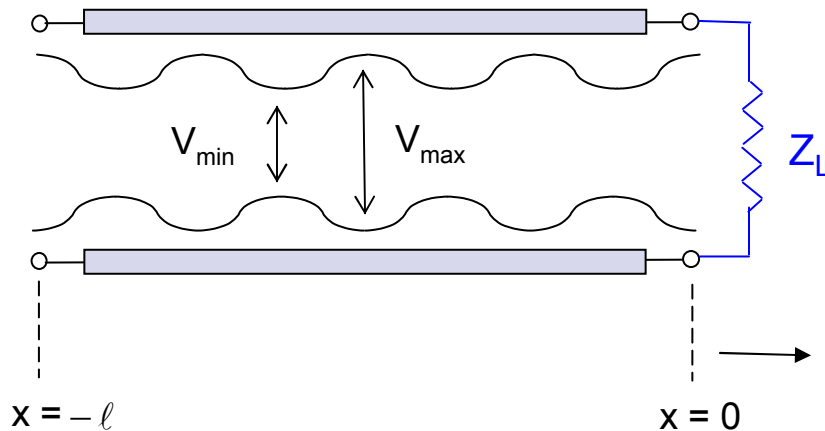

$$|V| = V_o^+ \sqrt{(1 + \rho)^2 - 4\rho \sin^2\left(\frac{\theta + 2\beta x}{2}\right)}$$

$$V_{\min} = V_o^+ \sqrt{(1 + \rho)^2 - 4\rho} = V_o^+ (1 - \rho)$$

$$V_{\max} = V_o^+ \sqrt{(1 + \rho)^2} = V_o^+ (1 + \rho)$$

$$\text{VSWR} \equiv \frac{V_{\max}}{V_{\min}} = \frac{1 + \rho}{1 - \rho} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

perfect match: $\rho = 0$, $\text{VSWR} = 1.0$


open / short: $\rho = 1$, $\text{VSWR} \rightarrow \infty$

It is an indicator on how well the load matches the line.

VSWR is the standing wave pattern INSIDE the line.


Only Γ at the reflected junction that counts


Exercise

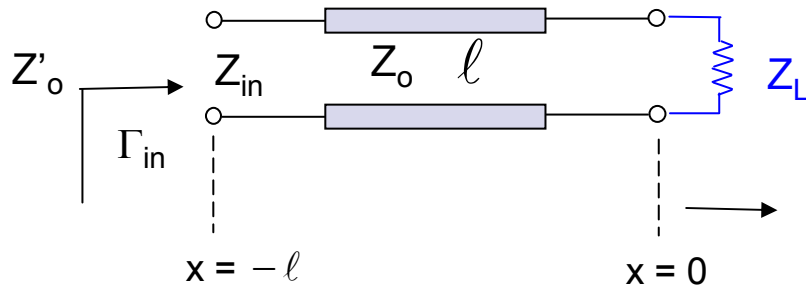

$Z_o = 50 \Omega$
 $Z'_o = 75 \Omega$
 $Z_L = 100 \Omega$
Length = $\lambda/8$
VSWR = ?

$\Gamma_L = 1/3$
VSWR = 2

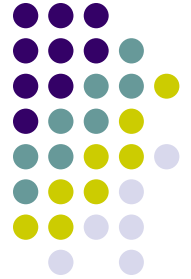

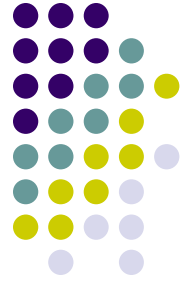

Return Loss

$$\text{RL} \equiv -20 \log \rho \quad (\text{dB})$$

perfect match: $\rho \rightarrow 0$, $\text{VSWR} \rightarrow 1.0$, $\text{RL} \rightarrow \infty$

open / short: $\rho = 1$, $\text{VSWR} \rightarrow \infty$, $\text{RL} \rightarrow 0 \text{ dB}$

$$\text{VSWR} \equiv \frac{1+\rho}{1-\rho} = \frac{1+|\Gamma|}{1-|\Gamma|} \longrightarrow \rho = |\Gamma| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}$$


Typical VSWR = 1.1 to 2
 $\rho = 0.048$ to 0.33
RL = 26 dB to 9.5 dB




Stub

Transmission line connecting nowhere(?)


- Open stub

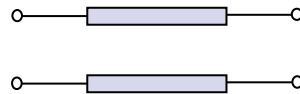


- Short stub

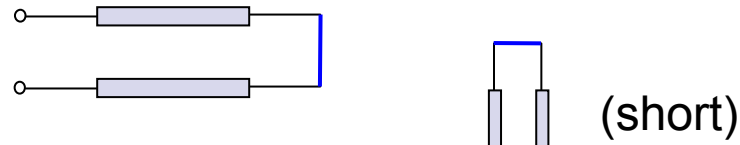

- Series stub


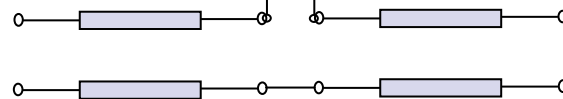


- Shunt stub

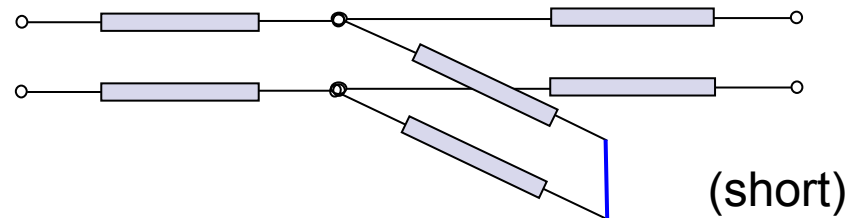




Open Shunt Stub

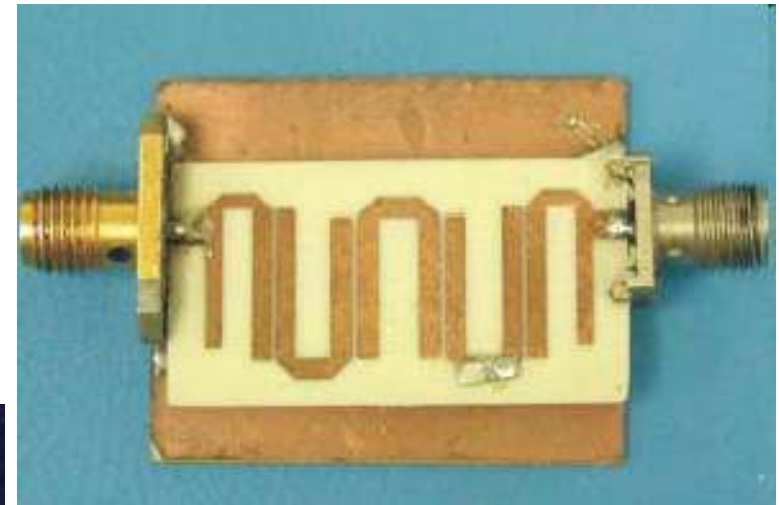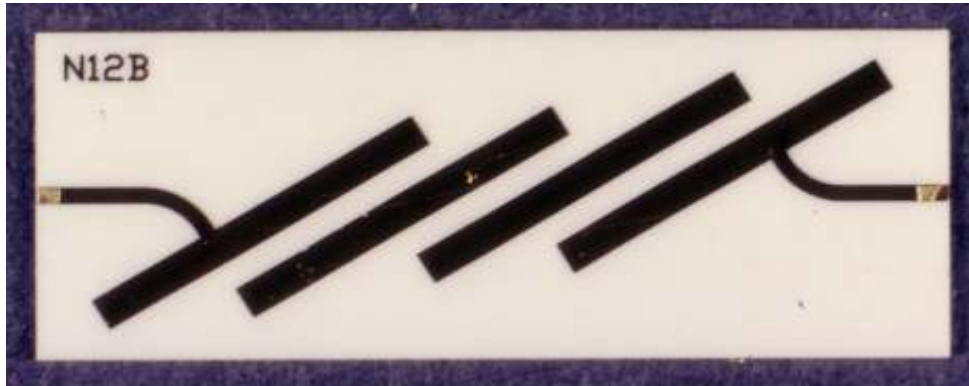

L-Band




Short Shunt Stub

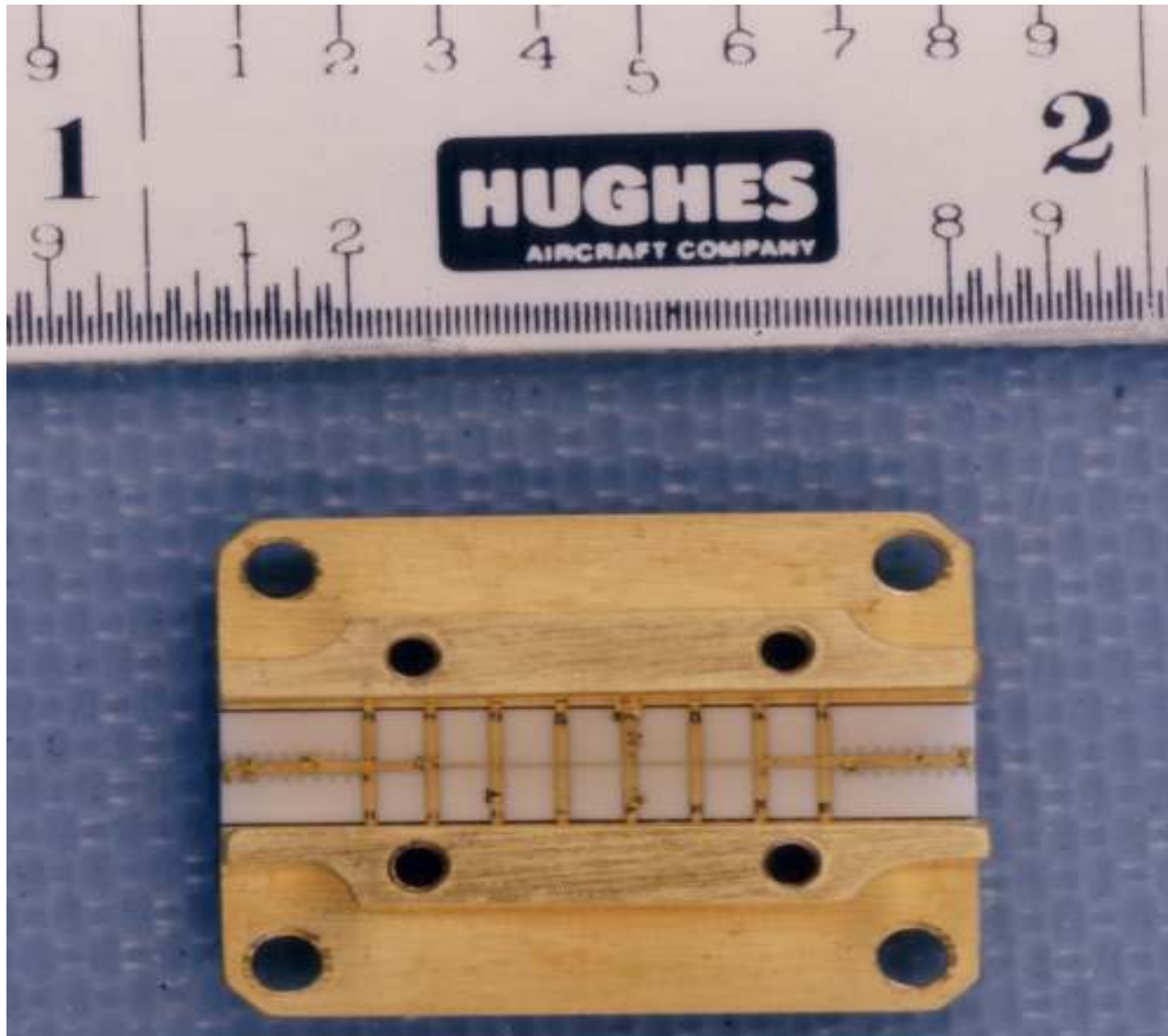

20 GHz
Interdigital
Filter


Radial Stub

18 GHz
Rat Race

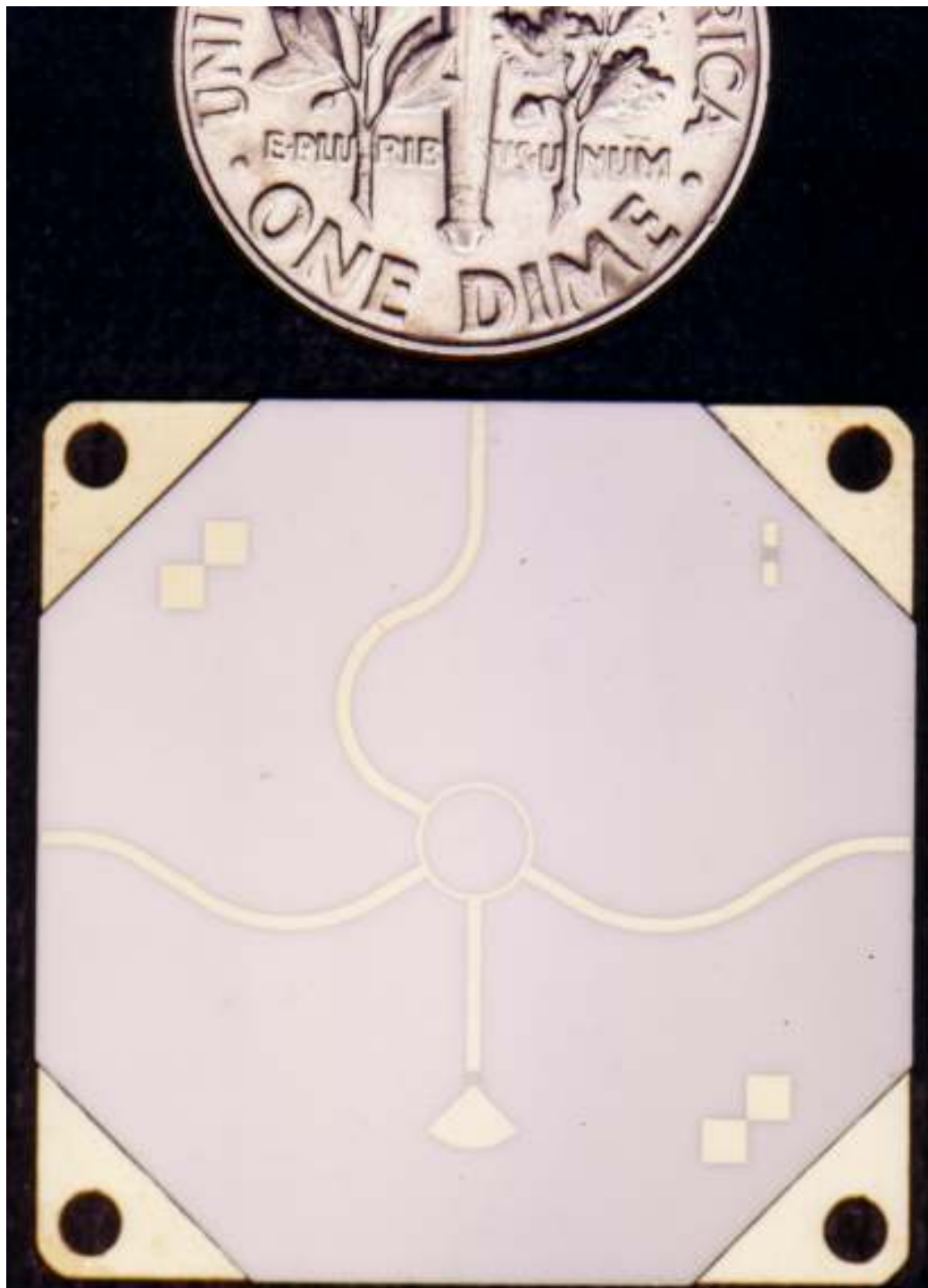





Tuning stub (open)

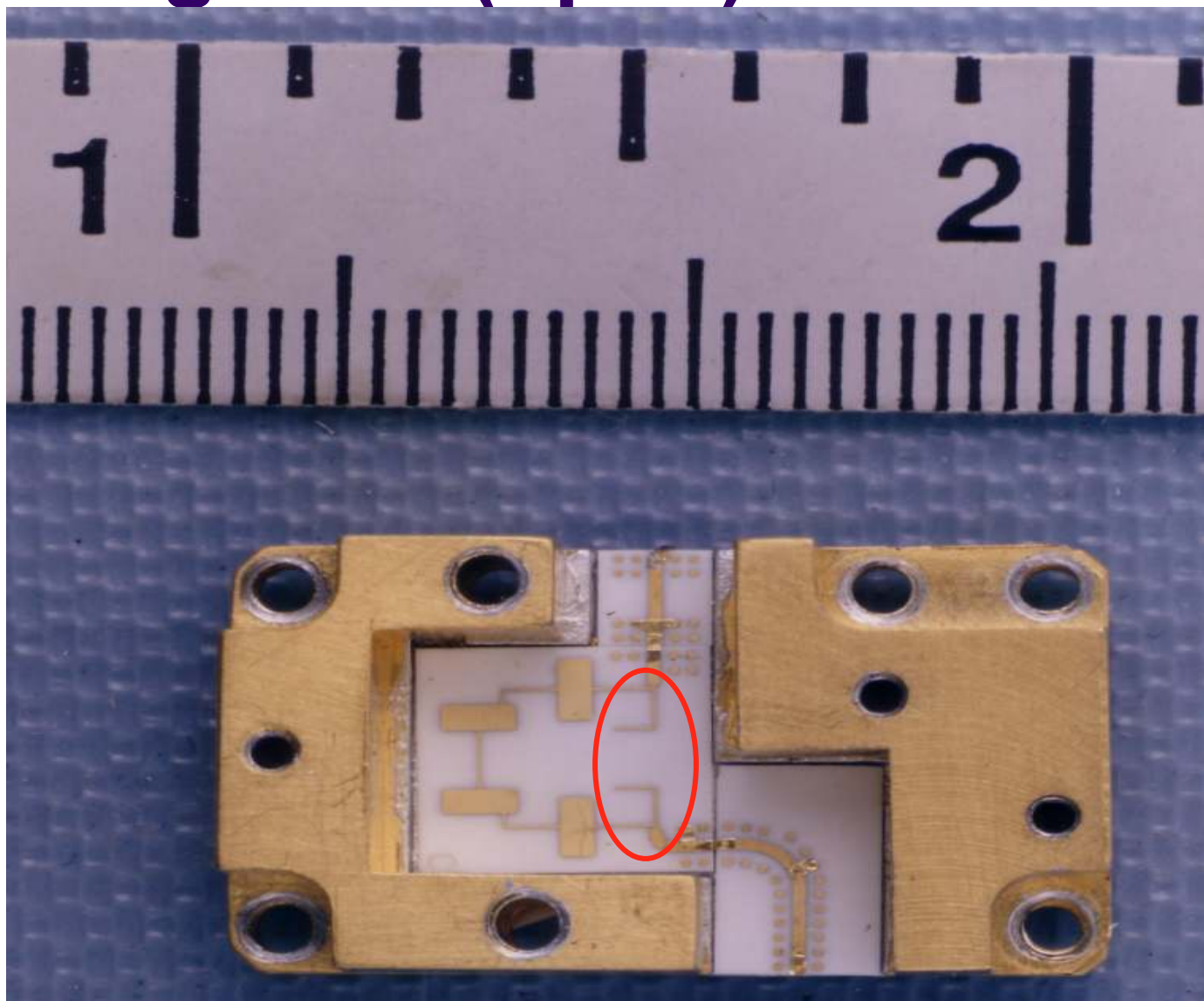




Short Stub

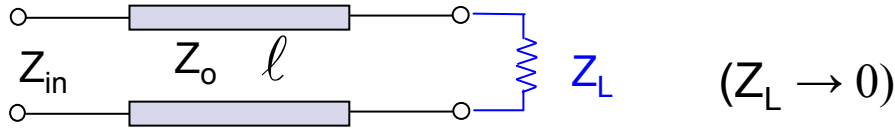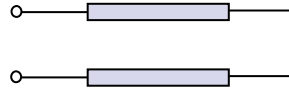

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$\bar{Z}_{sh} = j \tan \beta l$$
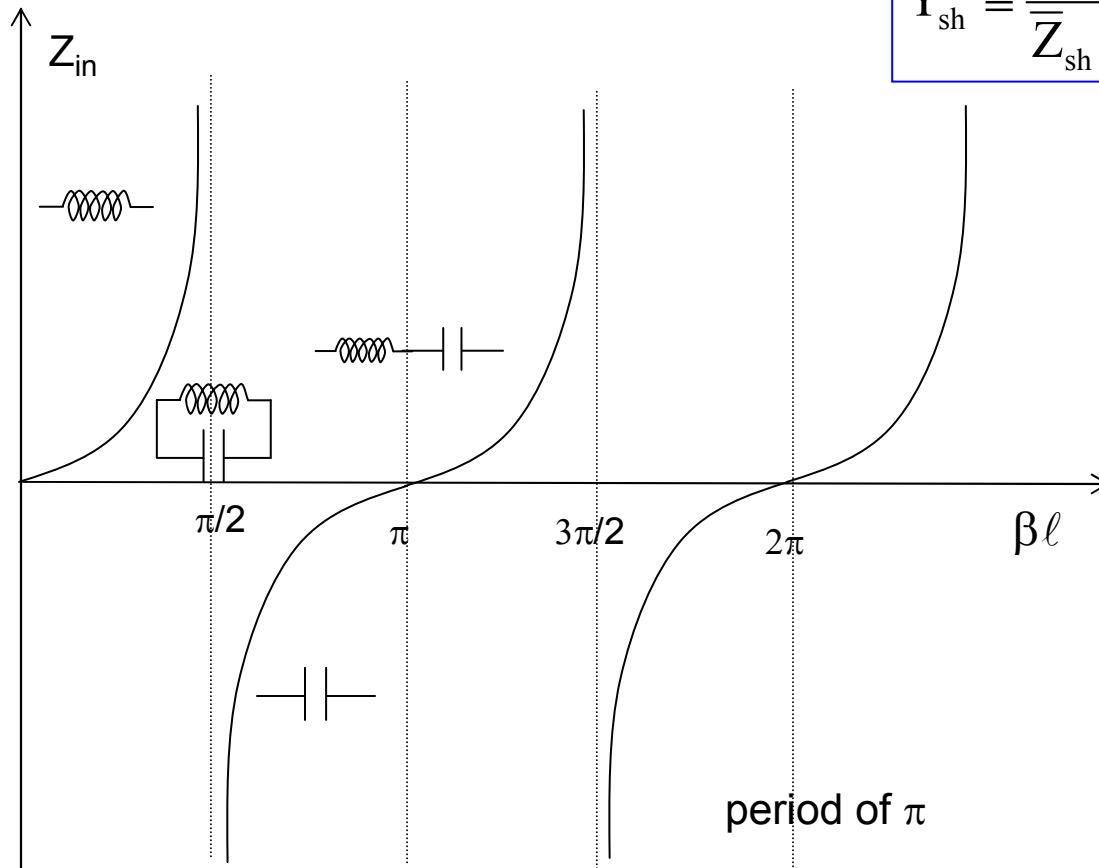
$$\bar{Y}_{sh} \equiv \frac{1}{\bar{Z}_{sh}} = -j \cot \beta l$$



$$Z_{coil} = j\omega L$$



$$Z_{cap} = -j/\omega C$$

$$Z_{sres} = j\omega L \left(1 - \frac{1}{\omega^2 LC} \right)$$

$$Z_{pres} = \frac{1}{j\omega C \left(1 - \frac{1}{\omega^2 LC} \right)}$$



Open Stub

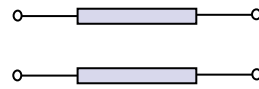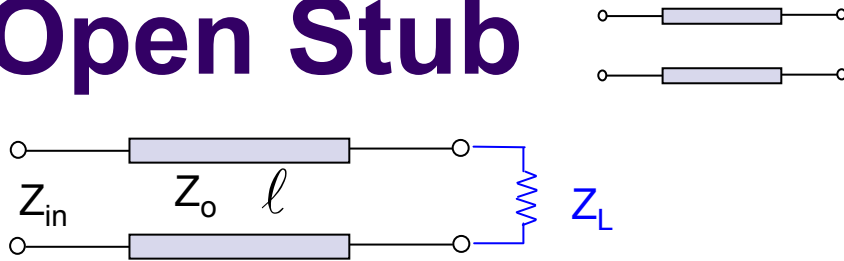


$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$(Z_L \rightarrow \infty)$

$$\bar{Z}_{op} = -j \cot \beta l$$

$$\bar{Y}_{op} = j \tan \beta l$$

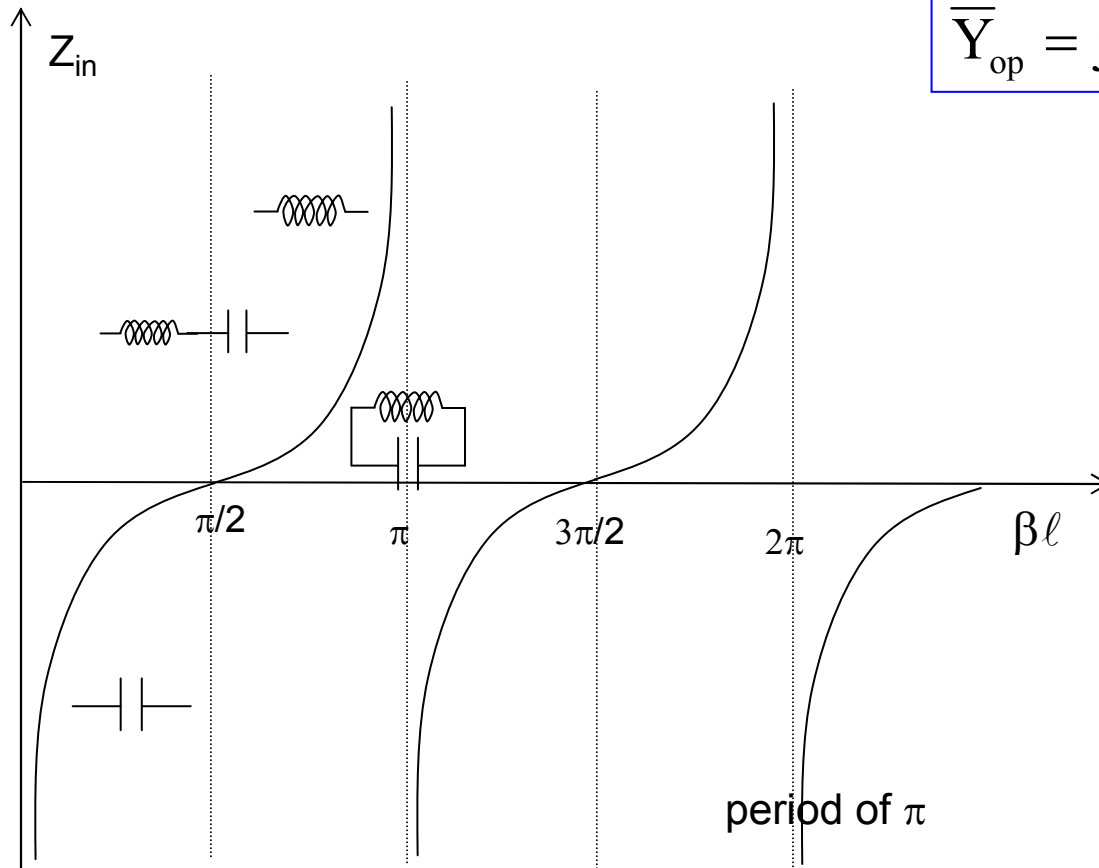

$$Z_{cap} = -j/\omega C$$


$$Z_{coil} = j\omega L$$

$$Z_{sres} = j\omega L \left(1 - \frac{1}{\omega^2 LC} \right)$$

$$Z_{pres} = \frac{1}{j\omega C \left(1 - \frac{1}{\omega^2 LC} \right)}$$





Exercise

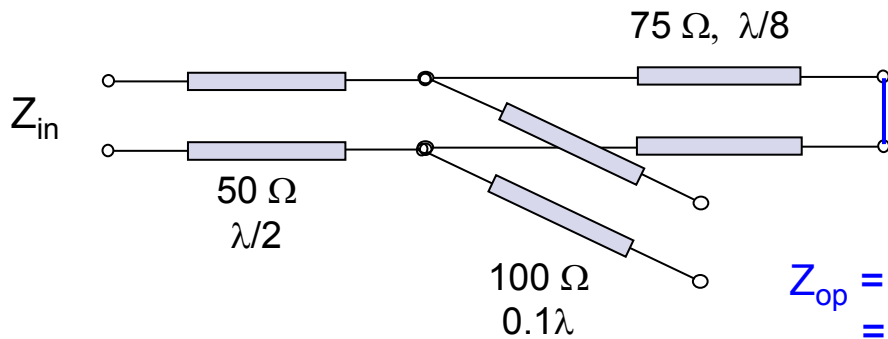

Find Z_{in} & Γ_{in} .

$$Z_{sh} = j Z_o \tan(\beta l) \\ = j 75 \tan(45^\circ) = j 75 \Omega$$
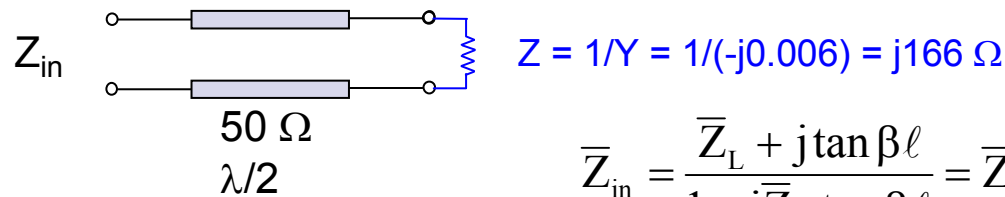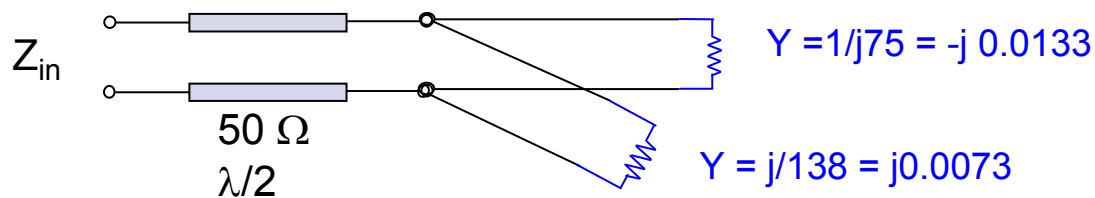
$$Z_{op} = -j Z_o \cot(\beta l) \\ = -j 100 \cot(36^\circ) = -j 138 \Omega$$



$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta \ell}{1 + j \bar{Z}_L \tan \beta \ell} = \bar{Z}_L$$

$$Z_{in} = j 166 \Omega$$

$$\Gamma_{in} = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{j166 - 50}{j166 + 50} = 1 \angle (107^\circ - 73^\circ) = 1 \angle 34^\circ$$



Admittance ($Y = 1/Z$)


$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$\bar{Y}_{in} \equiv \frac{1}{\bar{Z}_{in}} = \frac{1 + j \bar{Z}_L \tan \beta l}{\bar{Z}_L + j \tan \beta l}$$

$$\bar{Y}_{in} = \frac{1 + j(1/\bar{Y}_L) \tan \beta l}{1/\bar{Y}_L + j \tan \beta l}$$

$$\bar{Y}_{in} = \frac{\bar{Y}_L + j \tan \beta l}{1 + j \bar{Y}_L \tan \beta l}$$
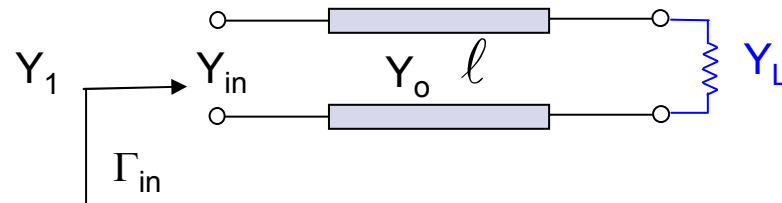
$$Y_{in} = Y_o \left(\frac{Y_L + j Y_o \tan \beta l}{Y_o + j Y_L \tan \beta l} \right)$$



$$\Gamma_{in} = \frac{Z_{in} - Z_1}{Z_{in} + Z_1}$$


$$\Gamma_{in} = \frac{1/Y_{in} - 1/Y_1}{1/Y_{in} + 1/Y_1}$$

$$\Gamma_{in} = \frac{Y_1 - Y_{in}}{Y_1 + Y_{in}} = \frac{1 - \bar{Y}_{in}}{1 + \bar{Y}_{in}}$$

useful for shunt circuits



Earlier exercise

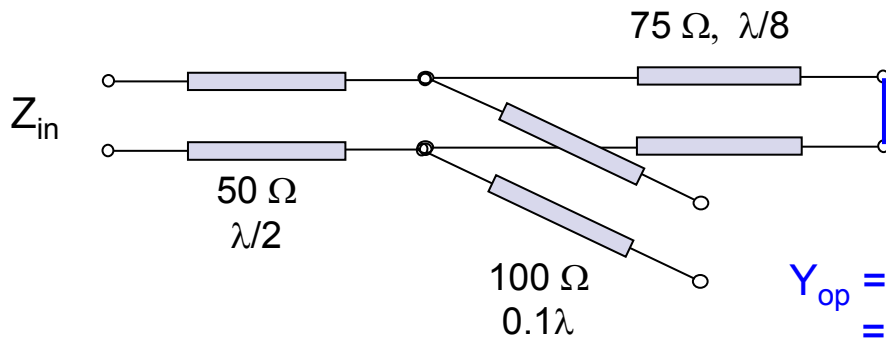



Find Z_{in} & Γ_{in} .

$$Y_{sh} = -j Y_o \cot(\beta l)$$

$$= -j (1/75) \cot(45^\circ) = -j 0.0133$$

$$Y_{op} = j Y_o \tan(\beta l)$$
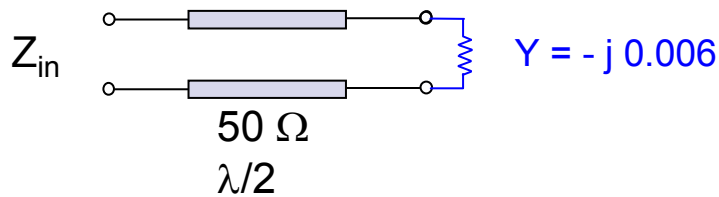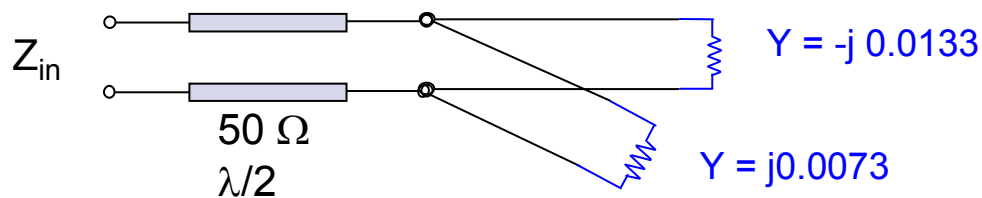
$$= j 0.01 \tan(36^\circ) = j 0.0073 \Omega$$



$$\bar{Y}_{in} = \frac{\bar{Y}_L + j \tan \beta \ell}{1 + j \bar{Y}_L \tan \beta \ell} = \bar{Y}_L$$


$$Y_L = -j 0.006$$

$$Z_{in} = j 166 \Omega$$

$$\Gamma_{in} = \frac{Y_o - Y_{in}}{Y_o + Y_{in}} = \frac{1/50 + j0.006}{1/50 - j0.006} = 1 \angle (17^\circ + 17^\circ) = 1 \angle 34^\circ$$



Earlier Exercise — power consideration

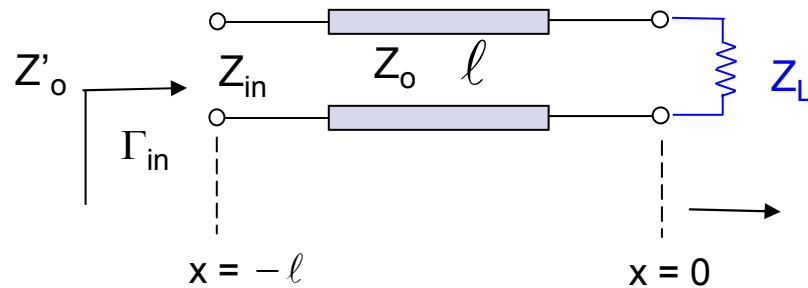

$$Z_o = 50 \Omega$$

$$Z'_o = 50 \Omega$$

$$Z_L = 100 \Omega$$

$$\text{Length} = \lambda/8$$

$$\Gamma_L = 1/3 \quad \Gamma_{in} = 1/3 (-90^\circ)$$

only change phase

$$\bar{Z}_{in} = \frac{\bar{Z}_L + j \tan \beta l}{1 + j \bar{Z}_L \tan \beta l}$$

$$Z_{in} = Z_o \left(\frac{Z_L + j Z_o \tan \beta l}{Z_o + j Z_L \tan \beta l} \right)$$

$$\Gamma_{in} = \frac{Z_{in} - Z'_o}{Z_{in} + Z'_o} = \frac{\bar{Z}'_{in} - 1}{\bar{Z}'_{in} + 1}$$

$$\text{Power reflected} = ? \quad \left| \frac{V^-}{V^+} \right|^2 = |\Gamma|^2 = \left| \frac{1}{3} \right|^2 = 11\%$$

$$\text{Power delivered} = ? \quad 1 - |\Gamma|^2 = 89\%$$

Don't double count reflection.... Γ_L & Γ_{in}


$$\text{Return Loss (RL)} = -20 \log |\rho| = +9.5 \text{ dB}$$




High f circuit elements




1 GHz lumped element
Band pass filter

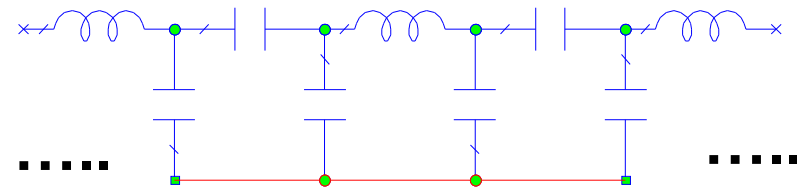

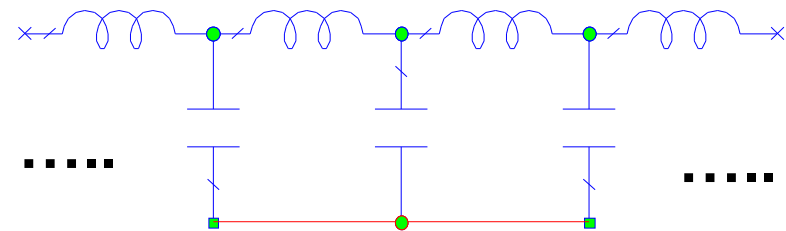
12 GHz lumped element
Low pass filter
much smaller



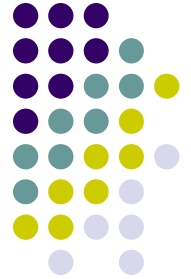A small loop of thin wire is an inductor !!



High-Z Line as inductor

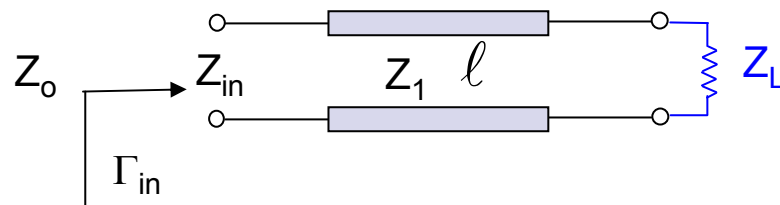


$$Z_{in} = Z_1 \left(\frac{Z_L + jZ_1 \tan \beta l}{Z_1 + jZ_L \tan \beta l} \right)$$

$Z_1 \gg Z_L$
 line length $< \lambda/4$ ($\pi/2$)
 $Z_L \sim Z_0$ (order of magnitude)

$$Z_{in} = Z_1 \left(\frac{a \angle + \Psi}{b \angle + \varphi} \right) = |Z_{in}| \angle + \theta$$

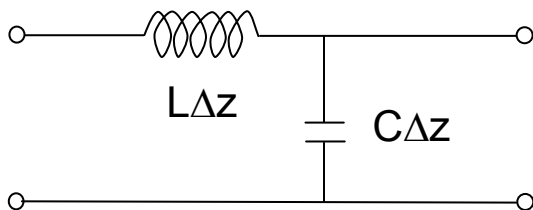
Z_{in} has a positive phase
 \rightarrow inductor-like !!!



small C, large L, series inductor



Low-Z Line as capacitor

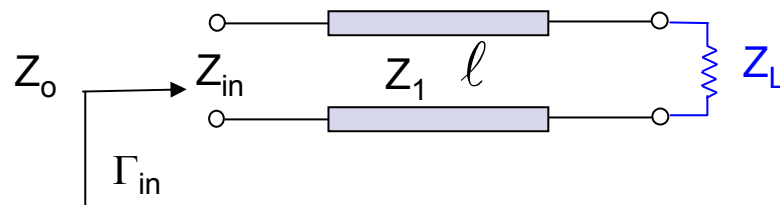


$$Z_{in} = Z_1 \left(\frac{Z_L + jZ_1 \tan \beta l}{Z_1 + jZ_L \tan \beta l} \right)$$

$Z_1 \ll Z_L$
 line length $\ll \lambda/4$ ($\pi/2$)
 $Z_L \sim Z_o$

$$Z_{in} = Z_1 \left(\frac{a \angle + \varphi}{b \angle + \Psi} \right) = |Z_{in}| \angle - \theta$$

$$Y_{in} = |Y_{in}| \angle + \theta$$

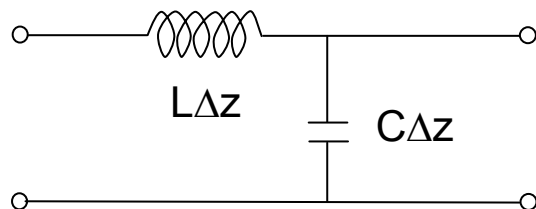
Y_{in} has a positive phase
 → capacitor-like !!!





small L, large C, shunt capacitor



Low pass filter

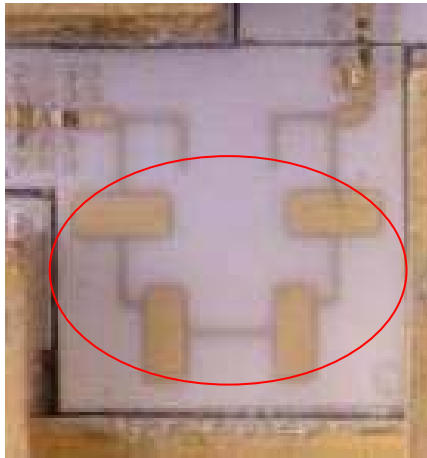

5 GHz low pass filter

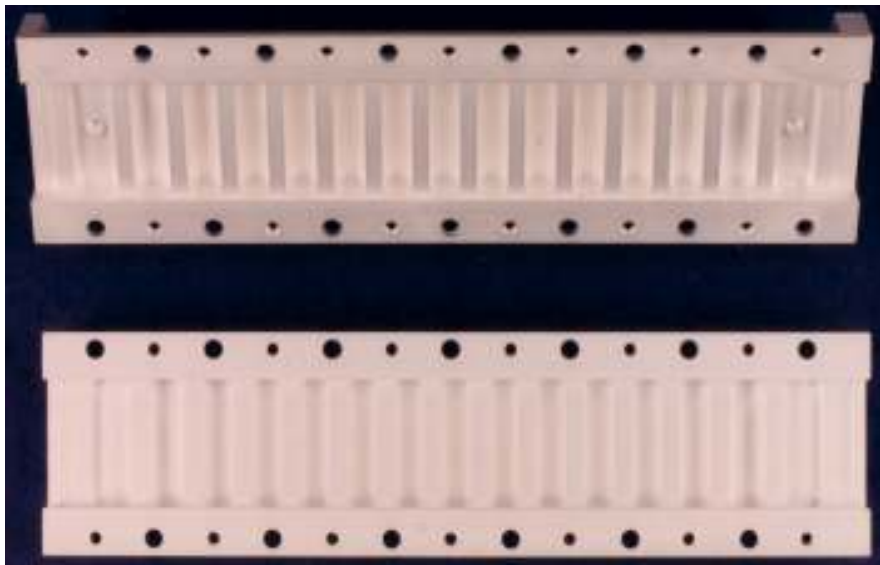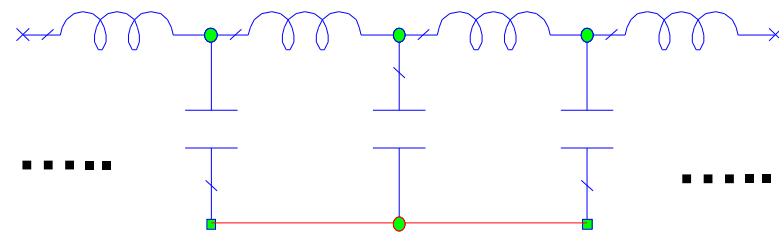



14 GHz low pass filter
high-low impedance lines
waveguide
high power
low loss



High-Low-Z lines



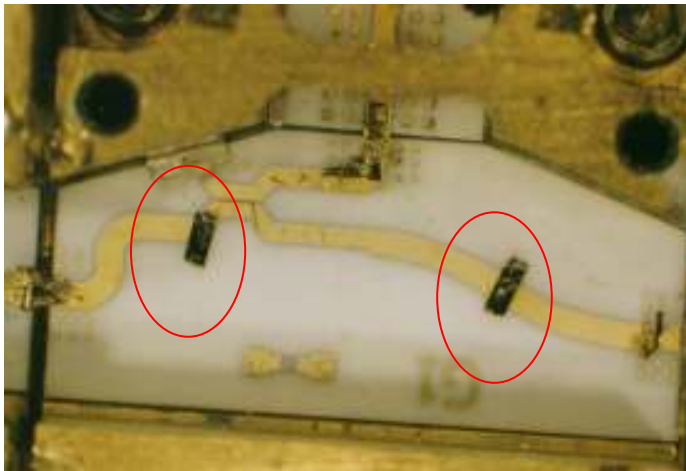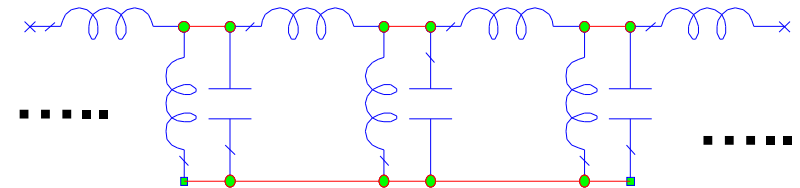20 GHz band pass filter
high Z lines \rightarrow inductors
Short shunt stubs $\lambda/4$ resonators




13 GHz coupler
Tuning with stubs (shunt open)
Think of them as shunt capacitors
 \rightarrow low Z lines



Homework

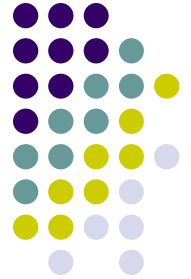1. A 100Ω transmission line has an effective dielectric constant of 1.65. Find the shortest open-circuited length of this line that appears at its input as a capacitor of 5 pF at 2.5 GHz . Repeat for an inductance of 5 nH .
2. A radio transmitter is connected to an antenna having an impedance $80 + j40 \Omega$ with a 50Ω coaxial cable. If the 50Ω transmitter can deliver 30 W when connected to a 50Ω load, how much power is delivered to the antenna?
3. A 75Ω coaxial transmission line has a length of 2 cm and is terminated with a load impedance of $37.5 + j75 \Omega$. If the dielectric constant of the line is 2.56 and the frequency is 3 GHz , find the input impedance to the line, the reflection coefficient at the load, the reflection coefficient at the input, and the SWR on the line.
4. The VSWR on a lossless 300Ω transmission line terminated in an unknown load impedance is 2.0, and the nearest voltage minimum is at a distance 0.3λ from the load. Determine (a) Γ_L , (b) Z_L .



5. Calculate VSWR, ρ , and return loss values to complete the entries in the following table.
6. Measurements on a 0.6 m lossless coaxial cable at 100 kHz show a capacitance of 54 pF when the cable is open-circuited, and an inductance of 0.30 μ H when it is short-circuited. (a) Determine Z_0 and ϵ_r of the medium.

VSWR	ρ	RL (dB)
1.00	0.00	∞
1.01		
	0.01	
1.05		32
		30
1.10		
1.20		
	0.10	
1.50		
		10
2.00		
2.50		